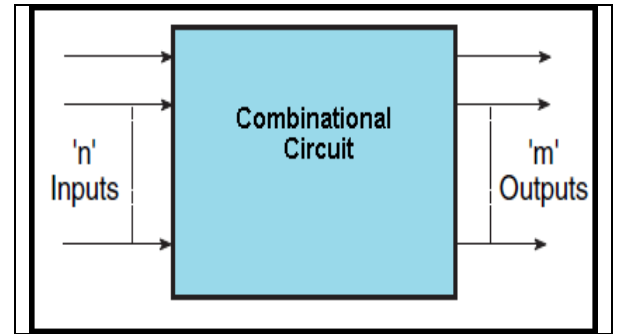


A **combinational circuit** is one where the output of that circuit at any time only depends on the present combination values of inputs. And the output is never depending on any past state value of input combination as well as the previous state output value. Now if we take any example then the logic gate is the most basic building block of combinational logic. Now as we know logic gates work according to the specified logic for specified gate. And those combinational circuits which are made by logic gate maintain Boolean



expression. In above see the block diagram of generalized combinational circuit. In above block diagram we can see that combinational logic circuit has “n” inputs that mean it can take 2^n combination of input values. The output “m” is depending on the Boolean expression of combinational logic circuit.

HALF-ADDER: As the name suggests *half-adder* is an arithmetic circuit block by using this circuit block we can be used to add two bits. As we know it can add two bit number so it has two inputs terminals (**A & B**) and as well as two outputs terminals, with one producing the SUM (**S**) output and the other producing the CARRY OUT (**C_{OUT}**).

TRUTH TABLE FOR HALF ADDER

A	B	S	C _{OUT}
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

K-map for **S**


A \ B	0	1
0	0	1
1	1	0

K-map for **C_{OUT}**


A \ B	0	1
0	0	0
1	0	1

Then for **S** we have $f(A, B) = \sum(1, 2) = \prod(0, 3)$ and **C_{OUT}** for we have $f(A, B) = \sum(3) = \prod(0, 1, 2)$

 
Then Sum (**S**) = $\bar{A}B + A\bar{B} = A \oplus B$ & Carry out (**C_{OUT}**) = AB



Half adder using X-OR and AND gates

 


Half adder using basic gates

 

NOTE THAT for
SUM $f(A, B) = \prod(0, 3)$
Then $S = (A + B)(\bar{A} + \bar{B})$

Half adder using NAND gates

 

Half adder using NOR gates

Full Adder: As we read early half adder can add only two bit of numbers so if we want to add two bit of input along with carry then we have to add three bits. But in half adder we can add only two bits so we need some extra. A *full adder* circuit is an arithmetic circuit block that can be used to add three bits to produce a SUM and a CARRY OUTPUT. By using full adder we can add large numbers because it can add two bit number with carry. Let us recall the procedure for adding larger binary numbers. We begin with the addition of LSBs of the forward to the next higher column bits. As a result, when we add the next adjacent higher column bits, we would be required to add three bits if there were a carry from the previous addition. We have a similar situation for the other higher column bits also until we reach the MSB. A full adder is therefore essential for the hardware implementation of an adder circuit capable of adding larger binary numbers. For full adder circuit the relation between input and output expressed by the Boolean expressions for the SUM(S) and CARRY OUTPUTS (C_{OUT})

TRUTH TABLE FOR FULL ADDER

C_{IN}	A	B	S	C_{OUT}
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

K-map for S

		$C_{in}A$			
		00	01	11	10
B	0	0	1	0	1
	1	1	0	1	0

K-map for C_{OUT}

		$C_{in}A$			
		00	01	11	10
B	0	0	0	1	0
	1	0	1	1	1

Then for S we have $f(C_{IN}, A, B) = \sum(1, 2, 4, 7) = \prod(0, 3, 5, 6)$ and C_{OUT} for we have $f(C_{IN}, A, B) = \sum(3, 5, 6, 7) = \prod(0, 1, 2, 4)$

From truth table $S = \sum m(1, 2, 4, 7) = \overline{C_{IN}} \overline{A} B + \overline{C_{IN}} A \overline{B} + C_{IN} \overline{A} \overline{B} + C_{IN} A B = \overline{C_{IN}} (\overline{A} B + A \overline{B}) + C_{IN} (\overline{A} \overline{B} + A B)$

$$= \overline{C_{IN}} (A \oplus B) + C_{IN} (A \odot B) = \overline{C_{IN}} (A \oplus B) + C_{IN} (\overline{A \oplus B}) = A \oplus B \oplus C_{IN}$$

Again $C_{OUT} = \sum m(3, 5, 6, 7) = \overline{C_{IN}} A B + C_{IN} \overline{A} B + C_{IN} A \overline{B} + A B C_{IN} = (\overline{A} B + A \overline{B}) C_{IN} + A B (\overline{C_{IN}} + C_{IN}) = (A \oplus B) C_{IN} + A B$


NOTE THAT

$$1. C_{OUT} = \sum m(3, 5, 6, 7) = \overline{C_{IN}} A B + C_{IN} \overline{A} B + C_{IN} A \overline{B} + A B C_{IN} = \overline{C_{IN}} A B + C_{IN} \overline{A} B + C_{IN} A \overline{B} + A B C_{IN} + A B C_{IN} + A B C_{IN} \\ = A B (C_{IN} + \overline{C_{IN}}) + C_{IN} B (A + \overline{A}) + C_{IN} A (B + \overline{B}) = A B + C_{IN} B + C_{IN} A.$$


$$2. \overline{C_{OUT}} = \overline{A B + C_{IN} B + C_{IN} A} = (\overline{A B}) \cdot (\overline{C_{IN} B}) \cdot (\overline{C_{IN} A}) = (\overline{A} + \overline{B}) (\overline{C_{IN}} + \overline{B}) (\overline{C_{IN}} + \overline{A}) = (\overline{A} \overline{C_{IN}} + \overline{A} \overline{B} + \overline{B} \overline{C_{IN}} + \overline{B}) (\overline{C_{IN}} + \overline{A}) \\ = \overline{A} \overline{C_{IN}} + \overline{A} \overline{C_{IN}} + \overline{A} \overline{B} \overline{C_{IN}} + \overline{A} \overline{B} + \overline{B} \overline{C_{IN}} + \overline{B} \overline{C_{IN}} \overline{A} + \overline{B} \overline{C_{IN}} + \overline{B} \overline{A} = \overline{A} \overline{B} + \overline{B} \overline{C_{IN}} (1 + \overline{A}) + \overline{A} \overline{C_{IN}} \\ = \overline{A} \overline{B} + \overline{C_{IN}} \overline{B} + \overline{C_{IN}} \overline{A}$$

$$3. \text{Again } (C_{IN} + A + B) \overline{C_{OUT}} + A B C_{IN} = C_{IN} \overline{C_{OUT}} + A \overline{C_{OUT}} + B \overline{C_{OUT}} + A B C_{IN} = C_{IN} \overline{A} \overline{B} + A \overline{C_{IN}} \overline{B} + B \overline{C_{IN}} \overline{A} + A B C_{IN} = S$$

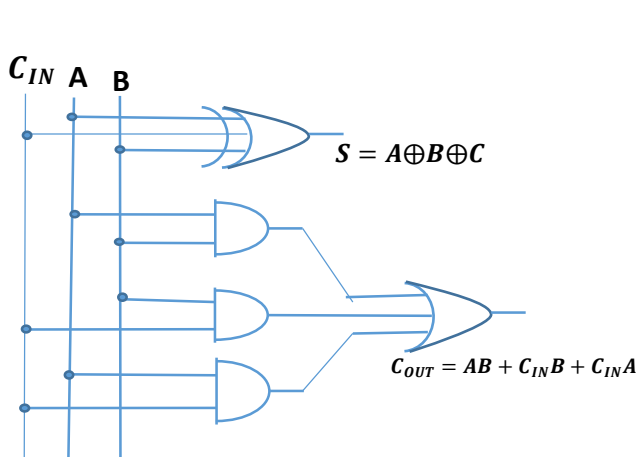
$$\text{Then } = (C_{IN} + A + B) \overline{C_{OUT}} + A B C_{IN}.$$



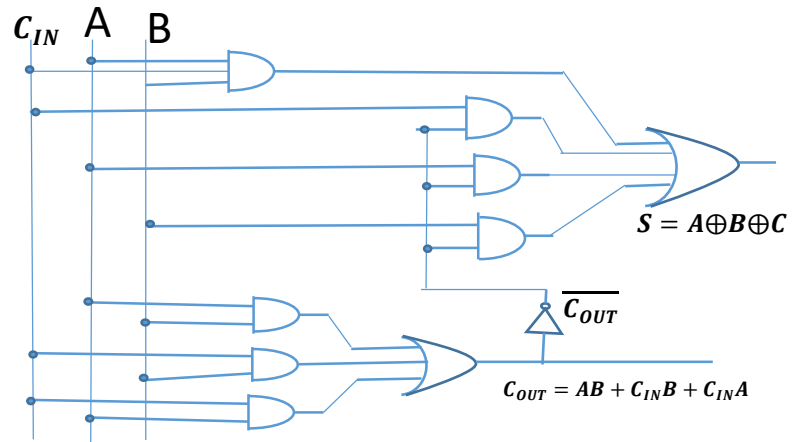
full adder using X-OR and AND and OR gates




Full adder using basic gates

 

Full adder using basic gates

 

Full adder using NAND gates

 

Full adder using NOR gates

HALF-SUBTRACTOR: As the name suggests *half-subtractor* is an arithmetic circuit block by using this circuit block we can be used to subtract two bits. As we know it can subtract two bit number so it has two inputs terminals (**A** & **B**) and as well as two outputs terminals, with one producing the DIFFERENCE (**D**) output and the other producing the BORROW OUT (**B_{OUT}**).

TRUTH TABLE FOR HALF ADDER

A	B	D	B _{OUT}
0	0	0	0
0	1	1	1
1	0	1	0
1	1	0	0

K-map for **D**


A \ B	0	1
0	0	1
1	1	0

K-map for **B_{OUT}**


A \ B	0	1
0	0	0
1	1	0

Then for **D** we have $f(A, B) = \sum(1, 2) = \prod(0, 3)$ and **B_{OUT}** for we have $f(A, B) = \sum(1) = \prod(0, 2, 3)$

 
Then **DIFFERENCE (D)** = $\bar{A}B + A\bar{B} = A \oplus B$ & **BORROW OUT (B_{OUT})** = $\bar{A}B$



 Half subtractor using X-OR and NOT and AND gates




Half subtractor using basic gates

 

NOTE THAT for DIFFERENCE $f(A, B) = \prod(0, 3)$

Then $D = (A + B)(\bar{A} + \bar{B})$

Half subtractor using NAND gates

 

Half subtractor using NOR gates

Full Subtractor: As we read early half subtractor can subtract only two bit of numbers so if we want to subtract two bit of input along with borrow then we have to subtract three bits. But in half subtractor we can subtract only two bits so we need some extra. A *full subtractor* circuit is an arithmetic circuit block that can be used to subtract three bits to produce a DIFFERENCE and a BORROW OUTPUT. By using full subtractor we can subtract large numbers because it can subtract two bit number with borrow. Let us recall the procedure for subtracting larger binary numbers. We begin with the subtraction of LSBs of the forward to the next higher column bits. As a result, when we subtract the next adjacent higher column bits, we would be required to subtract three bits if there were a borrow from the previous subtraction. We have a similar situation for the other higher column bits also until we reach the MSB. A full subtractor is therefore essential for the hardware implementation of an subtractor circuit capable of subtracting larger binary numbers. For full subtractor circuit the relation between input and output expressed by the Boolean expressions for the DIFFERENCE (**D**) and BORROW OUTPUTS (**B_{OUT}**)

TRUTH TABLE FOR FULL SUBTRACTOR

B_{IN}	A	B	D	B_{OUT}
0	0	0	0	0
0	0	1	1	1
0	1	0	1	0
0	1	1	0	0
1	0	0	1	1
1	0	1	0	1
1	1	0	0	0
1	1	1	1	1

K-map for **D**

D_{in}A					
B		00	01	11	10
		0	1	0	1
0	0	0	1	0	1
1	1	1	0	1	0

K-map for **B_{OUT}**

D_{in}A					
B		00	01	11	10
		0	0	0	1
0	0	0	0	0	1
1	1	1	0	1	1

Then for **D** we have $f(B_{IN}, A, B) = \sum(1, 2, 4, 7) = \prod(0, 3, 5, 6)$ and **B_{OUT}** for we have $f(B_{IN}, A, B) = \sum(1, 4, 5, 7) = \prod(0, 2, 3, 6)$

From truth table **D** = $\sum m(1, 2, 4, 7) = \overline{B}_{IN} \overline{A} B + \overline{B}_{IN} A \overline{B} + B_{IN} \overline{A} \overline{B} + B_{IN} A B = \overline{B}_{IN} (\overline{A} B + A \overline{B}) + B_{IN} (\overline{A} \overline{B} + A B)$

$$= \overline{B}_{IN} (A \oplus B) + B_{IN} (A \odot B) = \overline{B}_{IN} (A \oplus B) + B_{IN} (\overline{A \oplus B}) = A \oplus B \oplus B_{IN}$$

Again **B_{OUT}** = $\sum m(1, 4, 5, 7) = \overline{B}_{IN} \overline{A} B + B_{IN} \overline{A} \overline{B} + B_{IN} \overline{A} B + AB B_{IN} = (\overline{A} \overline{B} + AB) B_{IN} + \overline{A} B (\overline{B}_{IN} + B_{IN}) = (A \odot B) B_{IN} + \overline{A} B$


NOTE THAT

$$1. B_{OUT} = \sum m(1, 4, 5, 7) = \overline{B}_{IN} \overline{A} B + B_{IN} \overline{A} \overline{B} + B_{IN} \overline{A} B + AB B_{IN} = \overline{B}_{IN} \overline{A} B + B_{IN} \overline{A} \overline{B} + B_{IN} \overline{A} B + AB B_{IN} + AB B_{IN} + AB B_{IN} \\ = \overline{A} B (\overline{B}_{IN} + B_{IN}) + B_{IN} \overline{A} (\overline{B} + B) + B_{IN} B (A + \overline{A}) = \overline{A} B + B_{IN} \overline{A} + B_{IN} B.$$


$$2. \overline{B_{OUT}} = \overline{A} \overline{B} + B_{IN} \overline{B} + B_{IN} \overline{A} = (\overline{A} \overline{B}) \cdot (\overline{B_{IN} B}) \cdot (\overline{B_{IN} A}) = (A + \overline{B})(\overline{B_{IN}} + \overline{B})(\overline{B_{IN}} + A) = (A \overline{B_{IN}} + A \overline{B} + \overline{B} \overline{B_{IN}} + \overline{B})(\overline{B_{IN}} + A) \\ = A \overline{B_{IN}} + A \overline{B_{IN}} + A \overline{B} \overline{B_{IN}} + A \overline{B} + \overline{B} \overline{B_{IN}} + \overline{B} \overline{B_{IN}} A + \overline{B} \overline{B_{IN}} + \overline{B} A = A \overline{B} + \overline{B} \overline{B_{IN}} (1 + A) + A \overline{B_{IN}} \\ = A \overline{B} + \overline{B_{IN}} \overline{B} + A \overline{B_{IN}}$$

$$3. \text{Again } (\overline{B_{IN}} + A + \overline{B}) B_{OUT} + \overline{B_{IN}} A \overline{B} = \overline{B_{IN}} B_{OUT} + A B_{OUT} + \overline{B} B_{OUT} + \overline{B_{IN}} A \overline{B} = \overline{B_{IN}} \overline{A} B + AB_{IN} B + \overline{B} B_{IN} \overline{A} + \overline{B_{IN}} A \overline{B} = D$$

 
$$\text{Then } = (\overline{B_{IN}} + A + \overline{B}) B_{OUT} + \overline{B_{IN}} A \overline{B}.$$



 
full subtractor using X-OR and AND and OR gates



Full subtractor using basic gates

 


Full subtractor using NAND gates

 


Full subtractor using NOR gates

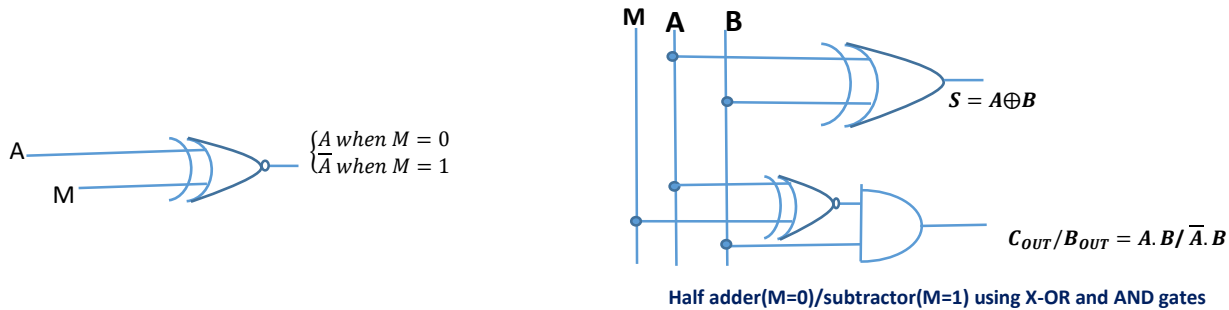HALF-ADDER//SUBTRACTOR: As X-OR gate can be used as an inverter when one of the input is high state for positive logic.



FULL ADDER//2's COMPLEMENT SUBTRACTOR:

 

DECODER : In [digital electronics](#), a **binary decoder** is a [combinational logic](#) circuit that converts binary information from the n coded inputs to a maximum of 2^n unique outputs.

They are used in a wide variety of applications, including data [demultiplexing](#), seven segment displays, and [memory](#) address decoding.

There are several types of binary decoders, but in all cases a decoder is an electronic circuit with multiple input and multiple output signals, which converts every unique combination of input states to a specific combination of output states. In addition to integer data inputs, some decoders also have one or more "enable" inputs. When the enable input is negated (disabled), all decoder outputs are forced to their inactive states.

Depending on its function, a binary decoder will convert binary information from n input signals to as many as 2^n unique output signals. Some decoders have less than 2^n output lines; in such cases, at least one output pattern will be repeated for different input values.

The simplest is the 1-to-2 line decoder. The truth table and the circuit are

The simplest is **the 1-to-2 line decoder (active HIGH output)**.
The truth table and the circuit are

A	O_1	O_0
0	0	1
1	1	0

The circuit diagram shows an input line labeled 'A'. This line branches into two paths. The first path goes through a NOT gate (represented by a triangle with a small circle at its tip) and then to an output labeled O_0 . The second path goes directly to an output labeled O_1 .


The simplest is **the 1-to-2 line decoder (active LOW output)**.
The truth table and the circuit are

A	O_1	O_0
0	1	0
1	0	1

The circuit diagram shows an input line labeled 'A'. This line branches into two paths. The first path goes through a NOT gate (represented by a triangle with a small circle at its tip) and then to an output labeled O_1 . The second path goes directly to an output labeled O_0 .


The 2-to-4 line decoder (active HIGH output).

E	A	B	O_3	O_2	O_1	O_0
1	0	0	0	0	0	1
1	0	1	0	0	1	0
1	1	0	0	1	0	0
1	1	1	1	0	0	0
0	X	X	0	0	0	0

 


The 2-to-4 line decoder (active LOW output).

E	A	B	O_3	O_2	O_1	O_0
0	0	0	1	1	1	0
0	0	1	1	1	0	1
0	1	0	1	0	1	1
0	1	1	0	1	1	1
1	X	X	1	1	1	1

 


The 3-to-8 line decoder (active HIGH output).

INPUTS			OUTPUTS							
A	B	C	O_7	O_6	O_5	O_4	O_3	O_2	O_1	O_0
0	0	0	0	0	0	0	0	0	0	1
0	0	1	0	0	0	0	0	0	1	0
0	1	0	0	0	0	0	0	1	0	0
0	1	1	0	0	0	0	1	0	0	0
1	0	0	0	0	0	1	0	0	0	0
1	0	1	0	0	1	0	0	0	0	0
1	1	0	0	1	0	0	0	0	0	0
1	1	1	1	0	0	0	0	0	0	0

 


The 3-to-8 line decoder (active LOW output).

INPUTS			OUTPUTS							
A	B	C	O_7	O_6	O_5	O_4	O_3	O_2	O_1	O_0
0	0	0	1	1	1	1	1	1	1	0
0	0	1	1	1	1	1	1	1	0	1
0	1	0	1	1	1	1	1	0	1	1
0	1	1	1	1	1	1	0	1	1	1
1	0	0	1	1	1	0	1	1	1	1
1	0	1	1	1	0	1	1	1	1	1
1	1	0	1	0	1	1	1	1	1	1
1	1	1	0	1	1	1	1	1	1	1

 


BCD to decimal decoder (active HIGH output).

INPUTS				OUTPUTS									
A	B	C	D	O_9	O_8	O_7	O_6	O_5	O_4	O_3	O_2	O_1	O_0
0	0	0	0	0	0	0	0	0	0	0	0	1	0
0	0	0	1	0	0	0	0	0	0	0	0	1	0
0	0	1	0	0	0	0	0	0	0	0	1	0	0
0	0	1	1	0	0	0	0	0	0	1	0	0	0
0	1	0	0	0	0	0	0	0	1	0	0	0	0
0	1	0	1	0	0	0	0	1	0	0	0	0	0
0	1	1	0	0	0	0	1	0	0	0	0	0	0
0	1	1	1	0	0	1	0	0	0	0	0	0	0
1	0	0	0	0	1	0	0	0	0	0	0	0	0
1	0	0	1	1	0	0	0	0	0	0	0	0	0

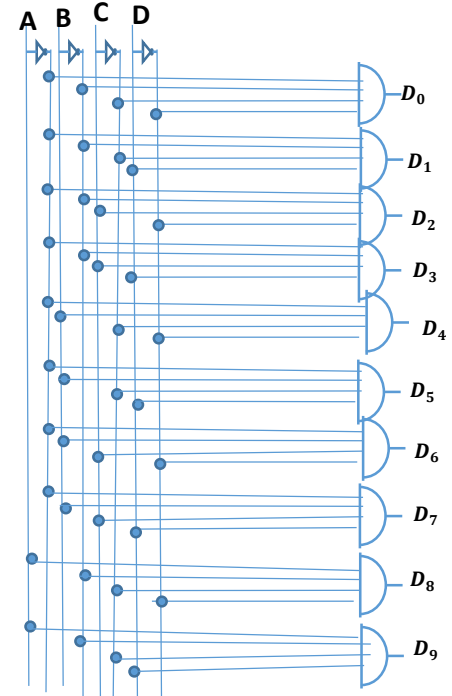

BCD to decimal decoder (active LOW output).


INPUTS				OUTPUTS									
A	B	C	D	O_9	O_8	O_7	O_6	O_5	O_4	O_3	O_2	O_1	O_0
0	0	0	0	1	1	1	1	1	1	1	1	1	0
0	0	0	1	1	1	1	1	1	1	1	1	0	1
0	0	1	0	1	1	1	1	1	1	1	0	1	1
0	0	1	1	1	1	1	1	1	1	0	1	1	1
0	1	0	0	1	1	1	1	1	0	1	1	1	1
0	1	0	1	1	1	1	1	0	1	1	1	1	1
0	1	1	0	1	1	1	0	1	1	1	1	1	1
0	1	1	1	1	1	0	1	1	1	1	1	1	1
1	0	0	0	1	0	1	1	1	1	1	1	1	1
1	0	0	1	0	1	1	1	1	1	1	1	1	1

 

CASCADING OF DECODER

3 to 8 Decoder using two 2 to 4 Decoder

INPUTS			OUTPUTS							
A	B	C	O_7	O_6	O_5	O_4	O_3	O_2	O_1	O_0
0	0	0	0	0	0	0	0	0	0	1
0	0	1	0	0	0	0	0	0	1	0
0	1	0	0	0	0	0	0	1	0	0
0	1	1	0	0	0	0	1	0	0	0
1	0	0	0	0	0	1	0	0	0	0
1	0	1	0	0	1	0	0	0	0	0
1	1	0	0	1	0	0	0	0	0	0
1	1	1	1	0	0	0	0	0	0	0

 

4 to 16 Decoder using two 3 to 8 Decoder

INPUTS				OUTPUTS															
A	B	C	D	O_{15}	O_{14}	O_{13}	O_{12}	O_{11}	O_{10}	O_9	O_8	O_7	O_6	O_5	O_4	O_3	O_2	O_1	O_0
0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	1
0	0	0	1	0	0	0	0	0	0	0	0	0	0	0	0	0	0	1	0
0	0	1	0	0	0	0	0	0	0	0	0	0	0	0	0	0	1	0	0
0	0	1	1	0	0	0	0	0	0	0	0	0	0	0	0	1	0	0	0
0	1	0	0	0	0	0	0	0	0	0	0	0	0	0	1	0	0	0	0
0	1	0	1	0	0	0	0	0	0	0	0	0	0	1	0	0	0	0	0
0	1	1	0	0	0	0	0	0	0	0	0	1	0	0	0	0	0	0	0
0	1	1	1	0	0	0	0	0	0	0	0	1	0	0	0	0	0	0	0
1	0	0	0	0	0	0	0	0	0	0	1	0	0	0	0	0	0	0	0
1	0	0	1	0	0	0	0	0	0	1	0	0	0	0	0	0	0	0	0
1	0	1	0	0	0	0	0	0	1	0	0	0	0	0	0	0	0	0	0
1	0	1	1	0	0	0	0	1	0	0	0	0	0	0	0	0	0	0	0
1	1	0	0	0	0	0	1	0	0	0	0	0	0	0	0	0	0	0	0
1	1	0	1	0	0	1	0	0	0	0	0	0	0	0	0	0	0	0	0
1	1	1	0	0	1	0	0	0	0	0	0	0	0	0	0	0	0	0	0
1	1	1	1	1	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0


The circuit diagram illustrates a 4-to-16 decoder implemented using two 3-to-8 decoders. The inputs are A, B, C, and D, where D is the most significant bit (MSB). The outputs are labeled O_{15} through O_0 .

Top 3-to-8 Decoder:

- Inputs: 2^0 (D), 2^1 (C), 2^2 (B).
- Enable (EN): Connected to A through an inverter.
- Outputs: O_{15} to O_8 .



Bottom 3-to-8 Decoder:

 - Inputs: 2^0 (D), 2^1 (C), 2^2 (B).
- Enable (EN): Connected to A through an inverter.
- Outputs: O_7 to O_0 .



Design combinational logic circuits for the logic function (i) $F(A, B, C, D) = \sum m(2, 4, 7, 9, 11)$

  (ii) $F(A, B, C, D) = \sum m(2, 4, 7, 9, 11)$ (iii) $F(A, B, C, D) = \sum m(10, 12, 14, 15)$





BINARY FULL ADDER USING DECODER

Truth table for full adder

C_{IN}	A	B	S	C_{OUT}
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

  Then for **S** we have $f(C_{IN}, A, B) = \sum(1, 2, 4, 7) = \prod(0, 3, 5, 6)$ and C_{OUT} for we have $f(C_{IN}, A, B) = \sum(3, 5, 6, 7) = \prod(0, 1, 2, 4)$



BCD to 7 segment display

BCD ([Binary Coded Decimal](#)) is an encoding scheme which represents each of the decimal numbers by its equivalent 4-bit binary pattern. [Seven segment displays](#) comprise of seven individual segments formed by either [Light Emitting Diodes](#) (LEDs) or Liquid Crystal Displays (LCDs) arranged in a definite pattern (Figure 1).

Decimal Digit	Input lines				Output lines							Display pattern
	A	B	C	D	a	b	c	d	e	f	g	
0	0	0	0	0	1	1	1	1	1	1	0	0
1	0	0	0	1	0	1	1	0	0	0	0	1
2	0	0	1	0	1	1	0	1	1	0	1	2
3	0	0	1	1	1	1	1	1	0	0	1	3
4	0	1	0	0	0	1	1	0	0	1	1	4
5	0	1	0	1	1	0	1	1	0	1	1	5
6	0	1	1	0	1	0	1	1	1	1	1	6
7	0	1	1	1	1	1	1	0	0	0	0	7
8	1	0	0	0	1	1	1	1	1	1	1	8
9	1	0	0	1	1	1	1	1	0	1	1	9

 
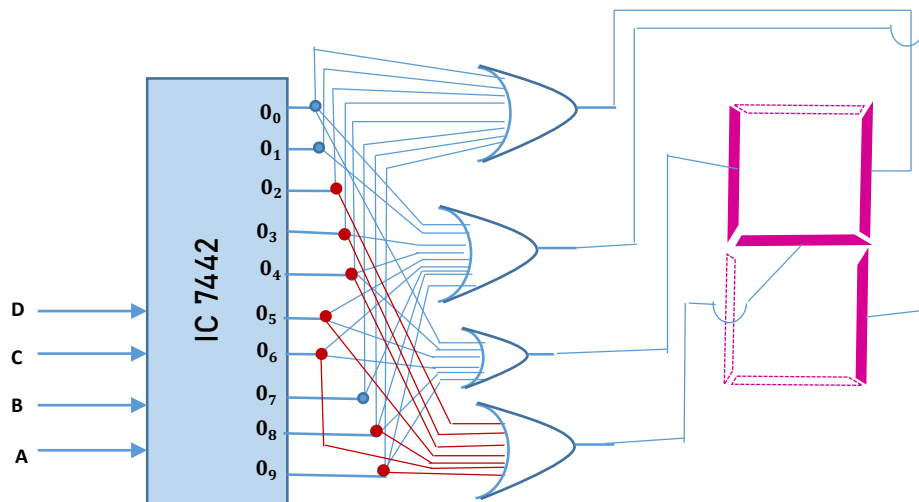
 


Figure1 Seven segment display

$$\begin{aligned}
 a &= F_1(A, B, C, D) = \sum m(0, 2, 3, 5, 6, 7, 8, 9) \\
 b &= F_2(A, B, C, D) = \sum m(0, 1, 2, 3, 4, 7, 8, 9) \\
 c &= F_3(A, B, C, D) = \sum m(0, 1, 3, 4, 5, 6, 7, 8, 9) \\
 d &= F_4(A, B, C, D) = \sum m(0, 2, 3, 5, 6, 8, 9) \\
 e &= F_5(A, B, C, D) = \sum m(0, 2, 6, 8, 9) \\
 f &= F_6(A, B, C, D) = \sum m(0, 4, 5, 6, 8, 9) \\
 g &= F_7(A, B, C, D) = \sum m(2, 3, 4, 5, 6, 8, 9).
 \end{aligned}$$


Displaying digit '4' using BCD to decimal decoder(IC 7442)**Displaying digit '4' using BCD to 7- segment Decoder(IC 7447)**

ENCODER: An **Encoder** is a combinational circuit that performs the reverse operation of Decoder. It has maximum of 2^n input lines and 'n' output lines. It will produce a binary code equivalent to the input, which is active High. Therefore, the encoder encodes 2^n input lines with 'n' bits. It is optional to represent the enable signal in encoders.

4 to 2 Encoder: Let 4 to 2 Encoder has four inputs I_3, I_2, I_1 & I_0 and two outputs O_1 & O_0 . The **block diagram** of 4 to 2 Encoder is shown in the following figure 1. At any time, only one of these 4 inputs can be '1' in order to get the respective binary code at the output.


The **Truth table** of 4 to 2 encoder is shown below.

Inputs				Outputs	
I_3	I_2	I_1	I_0	O_1	O_0
0	0	0	1	0	0
0	0	1	0	0	1
0	1	0	0	1	0
1	0	0	0	1	1

 

From truth table we get
 
$$O_0 = I_1 + I_3 \text{ \& } O_1 = I_2 + I_3$$



8 to 3 Encoder:



Inputs								Outputs		
I_7	I_6	I_5	I_4	I_3	I_2	I_1	I_0	O_2	O_1	O_0
0	0	0	0	0	0	0	1	0	0	0
0	0	0	0	0	0	1	0	0	0	1
0	0	0	0	1	0	0	0	0	1	0
0	0	0	1	0	0	0	0	1	0	1
0	0	1	0	0	0	0	0	1	1	0
0	1	0	0	0	0	0	0	1	1	1
1	0	0	0	0	0	0	0	1	1	1

from truth table we get

$$O_0 = I_1 + I_3 + I_5 + I_7$$

$$O_1 = I_2 + I_3 + I_6 + I_7$$

$$\& O_2 = I_4 + I_5 + I_6 + I_7$$

  

BCD Encoder:

Inputs										Outputs			
I_9	I_8	I_7	I_6	I_5	I_4	I_3	I_2	I_1	I_0	O_3	O_2	O_1	O_0
0	0	0	0	0	0	0	0	0	1	0	0	0	0
0	0	0	0	0	0	0	0	1	0	0	0	0	1
0	0	0	0	0	0	1	0	0	0	0	0	1	0
0	0	0	0	0	1	0	0	0	0	0	1	0	0
0	0	0	0	1	0	0	0	0	0	0	1	0	1
0	0	0	1	0	0	0	0	0	0	0	1	1	0
0	0	1	0	0	0	0	0	0	0	0	1	1	1
0	1	0	0	0	0	0	0	0	0	1	0	0	0
1	0	0	0	0	0	0	0	0	0	1	0	0	1



from truth table we get

$$O_0 = I_1 + I_3 + I_5 + I_7$$

$$O_1 = I_2 + I_3 + I_6 + I_7$$

$$\& O_2 = I_4 + I_5 + I_6 + I_7$$

$$\& O_3 = I_8 + I_9$$

  

PRIORITY ENCODER: A priority encoder provide n bits of binary coded output representing the position of the highest order active input of 2^n inputs. If two or more inputs are high at the same time, the input having the highest priority will take precedence.

4 to 2 priority encoder

A 4-to-2 priority encoder takes 4 input bits and produces 2 output bits. In this truth table, for all the non-explicitly defined input combinations (i.e. inputs containing 2, 3, or 4 high bits) the lower priority bits are shown as don't cares (X). Similarly when the inputs are 0000, the outputs are not valid and therefore they are XX. **Note that we take that I_3 have the highest priority and I_0 have lowest priority**

Truth table for 4:2 priority encoder					
Inputs				outputs	
I_3	I_2	I_1	I_0	O_1	O_0
0	0	0	0	X	X
0	0	0	1	0	0
0	0	1	X	0	1
0	1	X	X	1	0
1	X	X	X	1	1

K map for O_0

$I_3 I_2$	00	01	11	10
00	X	0	1	1
01	0	0	0	0
11	X	X	X	X
10	1	1	1	1

K map for O_1

$I_3 I_2$	00	01	11	10
00	X	0	0	0
01	1	1	1	1
11	1	1	1	1
10	1	1	1	1

Then $O_0 = I_3 + I_1 \bar{I}_2$ & $O_1 = I_3 + I_2$

PARITY GENERATOR AND PARITY CHECKER:

What is Parity Bit?

The parity generating technique is one of the most widely used error detection techniques for the data transmission. In digital systems, when binary data is transmitted and processed, data may be subjected to noise so that such noise can alter 0's (of data bits) to 1's and 1's to 0's.

Hence, **parity bit** is added to the word containing data in order to make number of 1's either even or odd. Thus it is used to detect errors, during the transmission of binary data. The message containing the data bits along with parity bit is transmitted from transmitter node to receiver node.

At the receiving end, the number of 1's in the message is counted and if it doesn't match with the transmitted one, then it means there is an error in the data.

Parity generator and checker

A parity generator is a combinational logic circuit that generates the parity bit in the transmitter. On the other hand, a circuit that checks the parity in the receiver is called parity checker. A combined circuit or devices of parity generators and parity checkers are commonly used in digital systems to detect the single bit errors in the transmitted data word.

The sum of the data bits and parity bits can be even or odd. In even parity, the added parity bit will make the total number of 1's an even amount whereas in odd parity the added parity bit will make the total number of 1's odd amount.

The basic principle involved in the implementation of parity circuits is that sum of odd number of 1's is always 1 and sum of even number of 1's is always zero. Such error detecting and correction can be implemented by using Ex-OR gates (since Ex-OR gate produce zero output when there are even number of inputs).


To produce two bits sum, one Ex-OR gate is sufficient whereas for adding three bits two Ex-OR gates are required as shown in below figure.

Even parity generator for two inputs			Odd parity generator for two inputs		
A	B	P	A	B	P
0	0	0	0	0	1
0	1	1	0	1	0
1	0	1	1	0	0
1	1	0	1	1	1

Even parity checker for two inputs

A	B	P	E
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1


Here $F(A, B, P) = \sum m(1, 2, 4, 7)$

 

Odd parity checker for two inputs

A	B	P	E
0	0	0	1
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	0

Here $F(A, B, P) = \sum m(0, 3, 5, 6)$

 

Even parity generator for three inputs

A	B	C	P
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

Here $F(A, B, P) = \sum m(1, 2, 4, 7)$



Odd parity generator for three inputs


A	B	C	P
0	0	0	1
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	0

Here $F(A, B, P) = \sum m(0, 3, 5, 6)$




Even parity checker for three inputs

A	B	C	P	E
0	0	0	0	0
0	0	0	1	1
0	0	1	0	1
0	0	1	1	0
0	1	0	0	1
0	1	0	1	0
0	1	1	0	0
0	1	1	1	1
1	0	0	0	1
1	0	0	1	0
1	0	1	0	0
1	0	1	1	1
1	1	0	0	0
1	1	0	1	1
1	1	1	0	1
1	1	1	1	0

 

Odd parity checker for three inputs

A	B	C	P	E
0	0	0	0	1
0	0	0	1	0
0	0	1	0	0
0	0	1	1	1
0	1	0	0	0
0	1	0	1	1
0	1	1	0	1
0	1	1	1	0
1	0	0	0	0
1	0	0	1	1
1	0	1	0	1
1	0	1	1	0
1	1	0	0	1
1	1	0	1	0
1	1	1	0	0
1	1	1	1	1

 

HOME TUSK (i) Even/ Odd parity generator for four inputs (ii) Even/ Odd parity checker for four inputs

Hints: (i) see Even parity checker for three inputs

